

CprE 381, Computer Organization and Assembly-Level Programming

Lab 2 Report

Student Name _____ Owen Jewell _____


Submit a typeset pdf version of this on Canvas by the due date. Refer to the highlighted language in the lab document for the context of the following questions.

[Part 0] Describe the provided DFF in dffg.vhd in terms of edge sensitivity and reset type (active low/high and synchronous/asynchronous).

The D flip flop in dffg.vhd is asynchronous reset and synchronous write. The edge sensitivity is rising edge because when the clock is 1 is when the output signal is changed to the value of D (input). The reset is active high because when the reset value is 1 it resets the output value to 0.

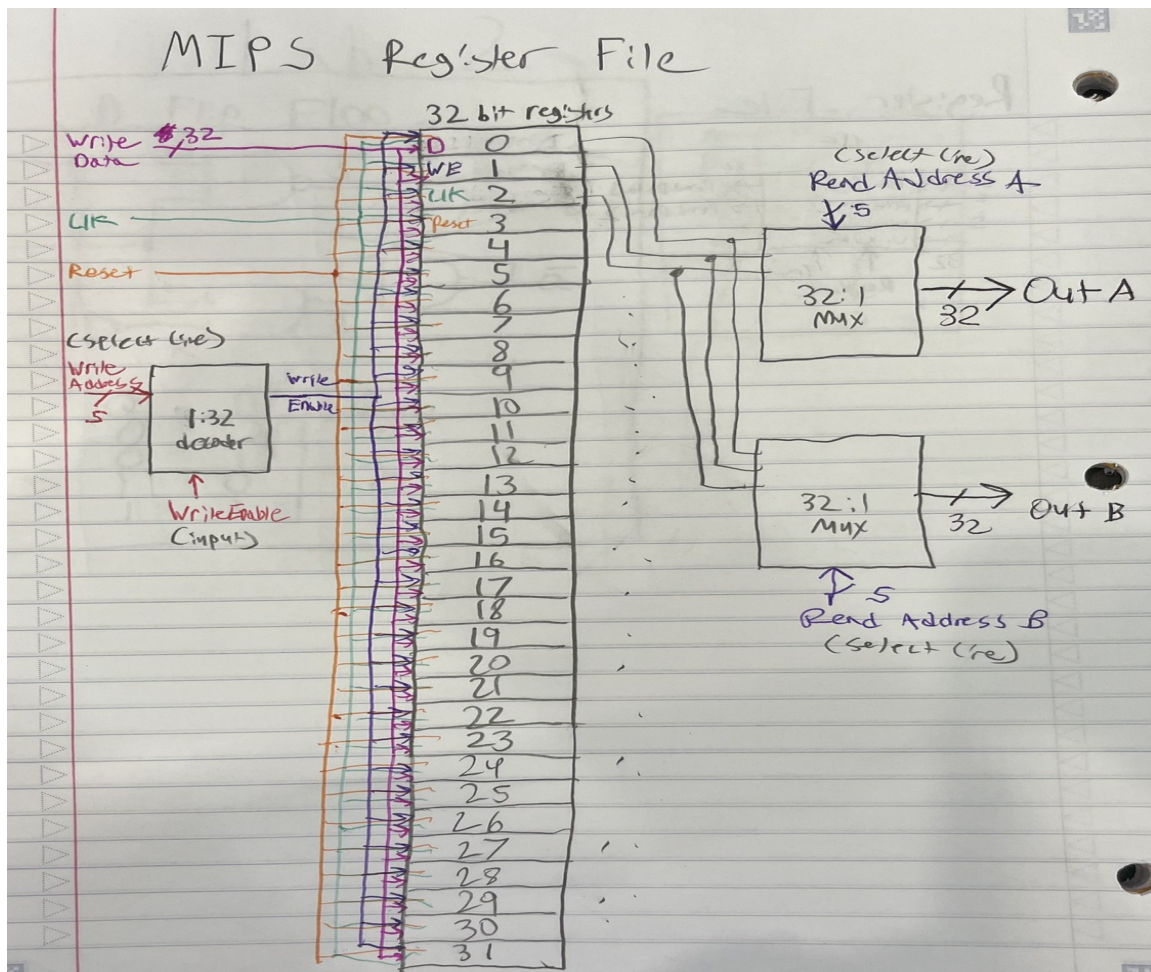[Part 2 (a)] Draw the interface description for the MIPS register file. Which ports do you think are necessary, and how wide (in bits) do they need to be?

(Decoder should say 5:32, its a 5 bit address select)




[Part 2 (b)] Create an N-bit register using this flip-flop as your basis.

```

14 L
15 library IEEE;
16 use IEEE.std_logic_1164.all;
17
18 entity register_N is
19 generic(N : integer := 32);
20 port(i_CLK : in std_logic;           -- Clock input
21      i_RST  : in std_logic;           -- Reset input
22      i_WE   : in std_logic;           -- Write enable input
23      i_WD   : in std_logic_vector(N-1 downto 0); -- Write Data value in
24      o_Q    : out std_logic_vector(N-1 downto 0)); -- Data value output
25 end register_N;
26
27 architecture structural of register_N is
28
29 component dffg is
30 port(i_CLK : in std_logic;
31      i_RST  : in std_logic;
32      i_WE   : in std_logic;
33      i_D    : in std_logic;
34      o_Q    : out std_logic);
35 end component;
36
37 begin
38
39 -- Instantiate N dffg instances.
40 G_NBit_DFFG: for i in 0 to N-1 generate
41 DFFGI_i: dffg port map(
42     i_CLK => i_CLK,
43     i_RST => i_RST,
44     i_WE  => i_WE,
45     i_D   => i_WD(i),
46     o_Q   => o_Q(i));
47 end generate G_NBit_DFFG;
48
49 end structural;
50
51

```


[Part 2 (c)] Waveform.

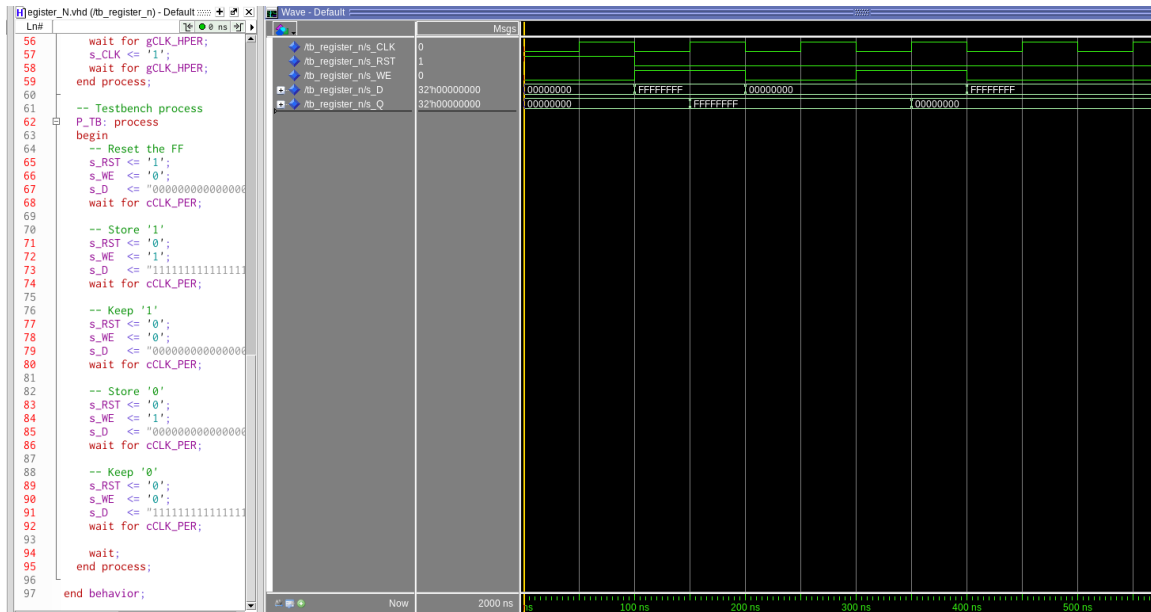

[Part 2 (d)] What type of decoder would be required by the MIPS register file and why?

The MIPS register file will need a 5:32 decoder because you need 5 bits to select registers 0-31.


[Part 2 (e)] Waveform.

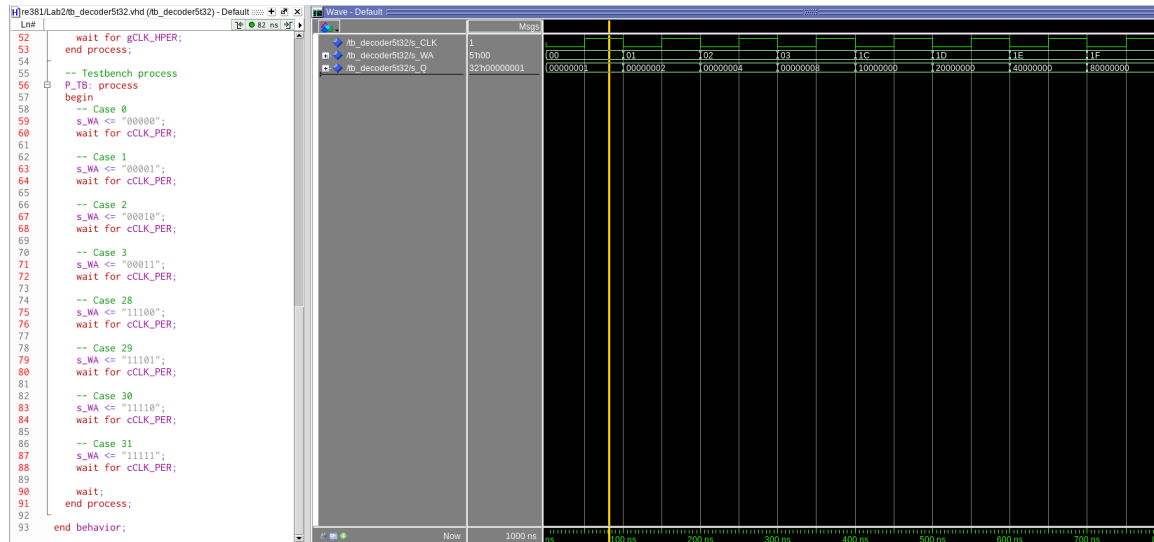

[Part 2 (f)] In your write-up, describe and defend the design you intend on implementing for the next part.

I am going to use the same strategy that I used for my 5:32 decoder for my 32:1 multiplexer. This strategy is one that I found in Free Range VHDL. The strategy is to use the dataflow method with the “with select then” statement. This statement allows me to assign a specific input vector to the output vector based on the 5 bit sleect.

[Part 2 (g)] Waveform.

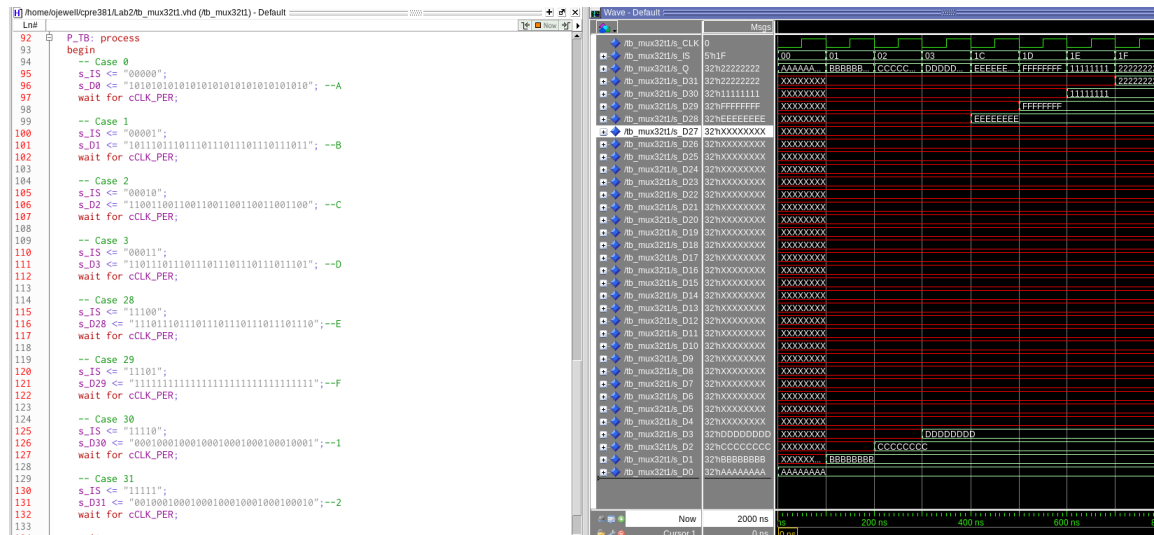

Although it may not look like it the waveform did work. I only assigned the first and last 4 in the test bench because they are in the statement so the middle ones will work if the ends do.

The diagram illustrates a 32-bit parallel adder implemented using a 32x32 ROM and two 32:1 multiplexers. The components and their connections are as follows:

- 32x32 ROM:** A central memory block with 32 inputs (labeled \$0 to \$31) and 32 outputs. It is controlled by a 5-bit **Write Address** and a **Write Enable** signal. It receives **Write Data** (32 bits) and is clocked by **Clk** and **Reset** signals.
- Write Address Decoder:** A 5-to-32 decoder that takes the 5-bit **Write Address** and enables one of the 32 ROM inputs (\$0 to \$31).
- Top 32:1 Multiplexer:** Selects one of the 32 ROM outputs to produce **Out A** (32 bits). Its select input is **Read Address A** (5 bits).
- Bottom 32:1 Multiplexer:** Selects one of the 32 ROM outputs to produce **Out B** (32 bits). Its select input is **Read Address B** (5 bits).

The screenshot displays a Verilog testbench simulation for a 32-bit register file. The left pane shows the Verilog code, and the right pane shows the simulation results.

Verilog Code (Left Pane):

```

Ln# | Code
--- | ---
59 | s_CLK <= '0';
60 | wait for gCLK_HPER;
61 | s_CLK <= '1';
62 | wait for gCLK_HPER;
63 | end process;
64 |
65 | -- Testbench process
66 | P_TB: process
67 | begin
68 |
69 |     -- Read from register 0 and register 0
70 |     s_WA <= "00000";
71 |     s_RA <= "00000";
72 |     s_RB <= "00000";
73 |     s_WE <= '0';
74 |     s_RST <= '0';
75 |     s_WD <= "00000000000000000000000000000000";
76 |
77 |     wait for cCLK_PER;
78 |
79 |     -- Write AAAAAAA to register 1
80 |     s_WA <= "00001";
81 |     s_RA <= "00000";
82 |     s_RB <= "00000";
83 |     s_WE <= '1';
84 |     s_RST <= '0';
85 |     s_WD <= "10101010101010101010101010101010";
86 |
87 |     wait for cCLK_PER;
88 |
89 |     -- Write BBBB BBBB to register 2
90 |     s_WA <= "00010";
91 |     s_RA <= "00000";
92 |     s_RB <= "00000";
93 |     s_WE <= '1';
94 |     s_RST <= '0';
95 |     s_WD <= "10111011101110111011101110111011";
96 |
97 |     wait for cCLK_PER;
98 |
99 |
100 |    -- Read from register 1 and register 2
101 |    s_WA <= "00000";
102 |    s_RA <= "00001";
103 |    s_RB <= "00010";
104 |    s_WE <= '0';
105 |    s_RST <= '0';
106 |    s_WD <= "00000000000000000000000000000000";
107 |

```


Simulation Results (Right Pane):

The right pane shows the simulation results for the register file's outputs. The signals are listed in the left column, and their values are shown in the right column. The signals are:


- nb_registerfile/s_CLK**: 1
- nb_registerfile/s_RST**: 0
- nb_registerfile/s_WE**: 0
- nb_registerfile/s_WD**: 32'h00000000
- nb_registerfile/s_OA**: 32'hAAAAAAA
- nb_registerfile/s_OB**: 32'hBBBBBBBB
- nb_registerfile/s_WA**: 5'h00
- nb_registerfile/s_RA**: 5'h01
- nb_registerfile/s_RB**: 5'h02

The right column shows the values of the signals over time. The signals are shown in hexadecimal and binary. The values are:

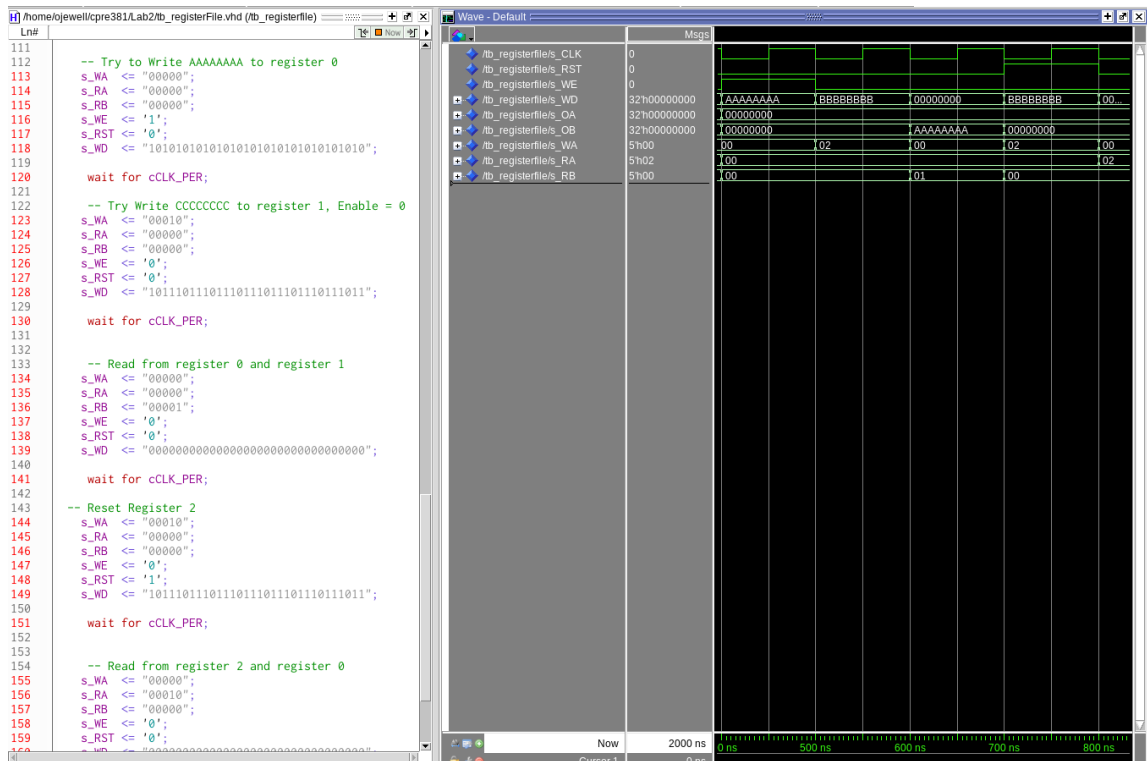
- nb_registerfile/s_CLK**: 1
- nb_registerfile/s_RST**: 0
- nb_registerfile/s_WE**: 0
- nb_registerfile/s_WD**: 000...AAA...BBB...00000000
- nb_registerfile/s_OA**: 00000000...AAAAAAA
- nb_registerfile/s_OB**: 00000000...BBBBBBBB
- nb_registerfile/s_WA**: 00...01...02...00
- nb_registerfile/s_RA**: 00...01...01...00
- nb_registerfile/s_RB**: 00...02...02...00



 [Part 3 (b)] Draw a symbol for this MIPS-like datapath.




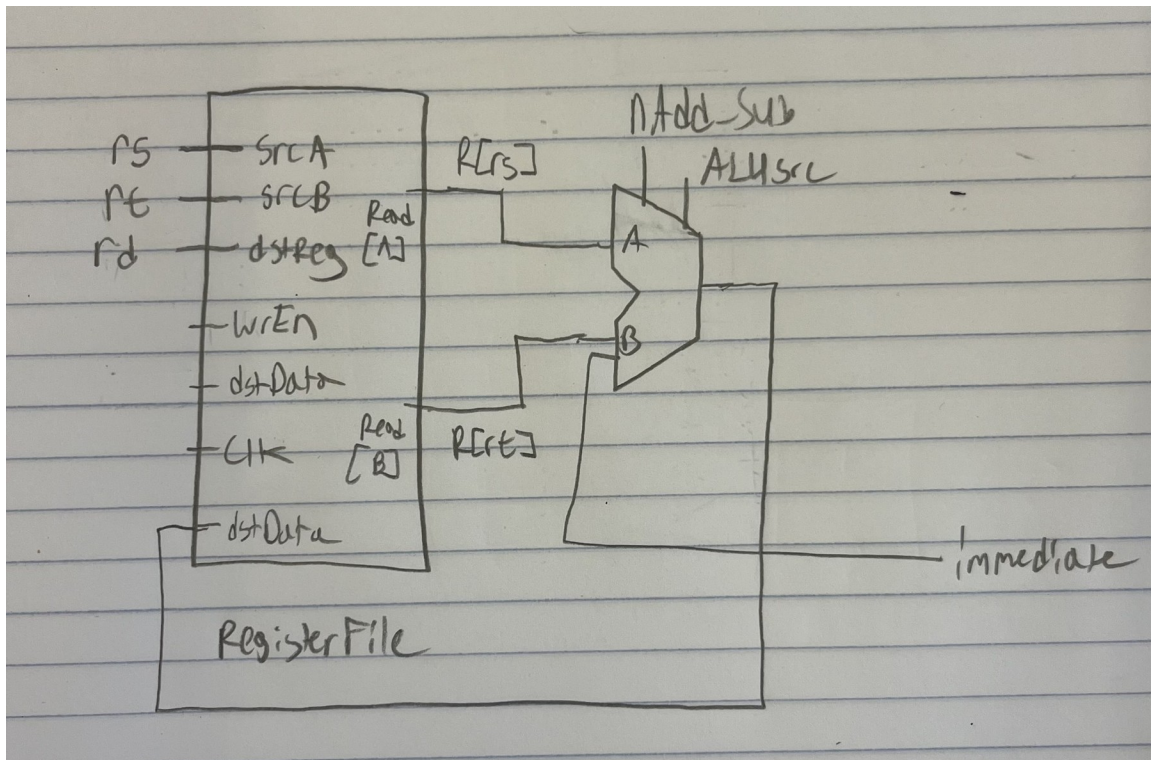[Part 3 (c)] Draw a schematic of the simplified MIPS processor datapath consisting only of the component described in part (a) and the register file from problem (1).



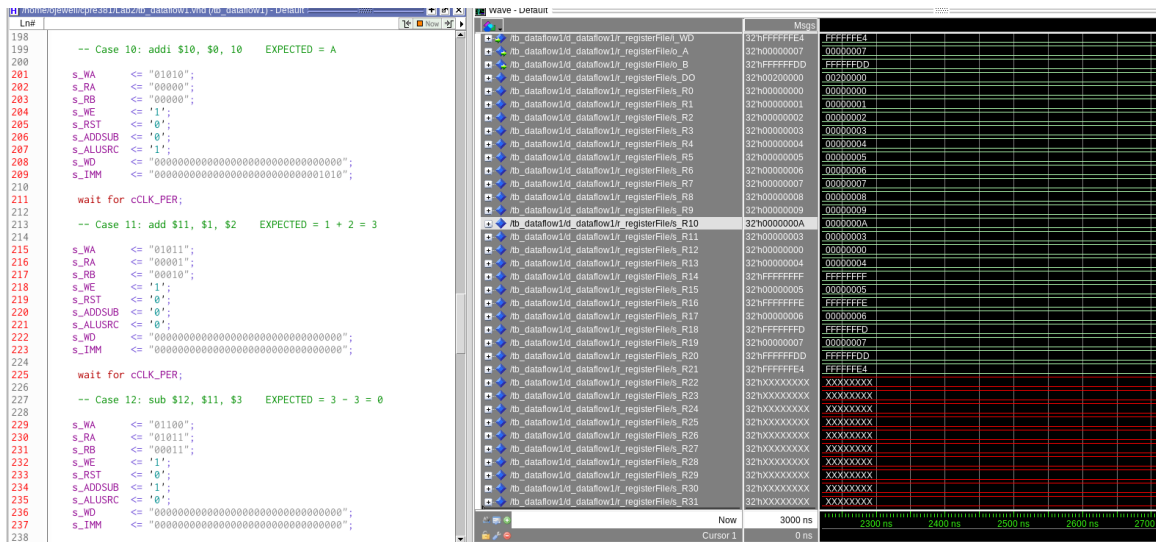[Part 3 (d)] Include in your report waveform screenshots that demonstrate your properly functioning design. Annotate what the final register file state should be.

- Case 1: addi \$1, \$0, 1 EXPECTED = 1
- Case 2: addi \$2, \$0, 2 EXPECTED = 2
- Case 3: addi \$3, \$0, 3 EXPECTED = 3
- Case 4: addi \$4, \$0, 4 EXPECTED = 4
- Case 5: addi \$5, \$0, 5 EXPECTED = 5
- Case 6: addi \$6, \$0, 6 EXPECTED = 6
- Case 7: addi \$7, \$0, 7 EXPECTED = 7
- Case 8: addi \$8, \$0, 8 EXPECTED = 8
- Case 9: addi \$9, \$0, 9 EXPECTED = 9
- Case 10: addi \$10, \$0, 10 EXPECTED = A
- Case 11: add \$11, \$1, \$2 EXPECTED = 1 + 2 = 3
- Case 12: sub \$12, \$11, \$3 EXPECTED = 3 - 3 = 0
- Case 13: add \$13, \$12, \$4 EXPECTED = 0 + 4 = 4
- Case 14: sub \$14, \$13, \$5 EXPECTED = 4 - 5 = -1 (FFFFFFF)
- Case 15: add \$15, \$14, \$6 EXPECTED = -1 + 6 = 5
- Case 16: sub \$16, \$15, \$7 EXPECTED = 5 - 7 = -2 (FFFFFFFE)
- Case 17: add \$17, \$16, \$8 EXPECTED = -2 + 8 = 6
- Case 18: sub \$18, \$17, \$9 EXPECTED = 6 - 9 = -3 (FFFFFFFD)
- Case 19: add \$19, \$18, \$10 EXPECTED = -3 + 10 = 7
- Case 20: addi \$20, \$0, -35 EXPECTED = -35 (FFFFFFDD)
- Case 21: add \$21, \$19, \$20 EXPECTED = 7 + -35 = -22 (FFFFFFE4)




As can be seen in the screenshot all of the actual register values match the expected

[Part 4 (a)] Read through the mem.vhd file, and based on your understanding of the VHDL implementation, provide a 2-3 sentence description of each of the individual ports (both generic and regular).

The generic section of the memory entity contains the definitions for two different size vectors. The first, data_width is of size 32 and will be used to represent the actual words being stored in memory. The second, addr_width, is of size 10 and is the width of the address in memory.

The port section contains 4 in ports and 5 out ports. The clk port is an in port that will represent the clock cycle. Data will be stored in memory on the positive edge of the clock. This is handled by the rising edge clock cycle. The second port is the addr port which is also an in port. The addr value is an unsigned value used to access a specific address in memory. The data port is in the third in port. This 32 bit vector will be used to store words in memory. The last in port is the we port. This is the write enable port. If this std_logic value is a 1 then data can be stored in memory, but if it is a 0 then data cannot be written. The last port is the q port which is the output port. This 32 bit vector will be used when data is being read from memory.

[Part 4 (c)] Waveforms.

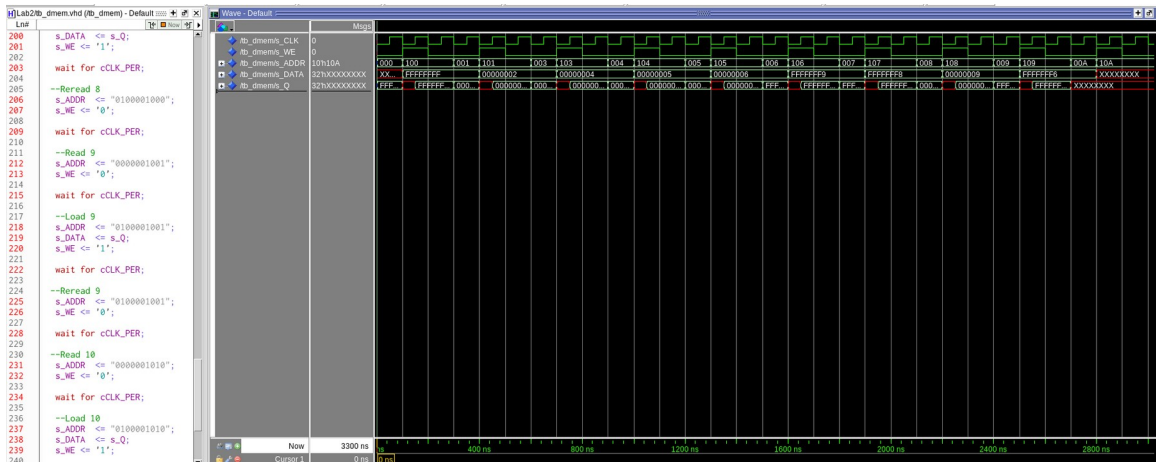

[Part 5 (a)] What are the MIPS instructions that require some value to be sign extended? What are the MIPS instructions that require some value to be zero extended?


Addi, addiu, lbu, lhu, ll, lw, slti, sltiu, sb, sc, sh, sw all require a value to be sign extended.

Andi, ori, require a value to be zero extended.

[Part 5 (b)] what are the different 16-bit to 32-bit “extender” components that would be required by a MIPS processor implementation?

First the component needs to check the 1 bit select that indicates either a 0 extend or a sign extend. If it is a 0 extend it is pretty simple to iterate through bits 16-31 and add 0's. Else if it is a sign extend you iterate through bits 16-31 and set them to input bit 15).

[Part 5 (d)] Waveform.

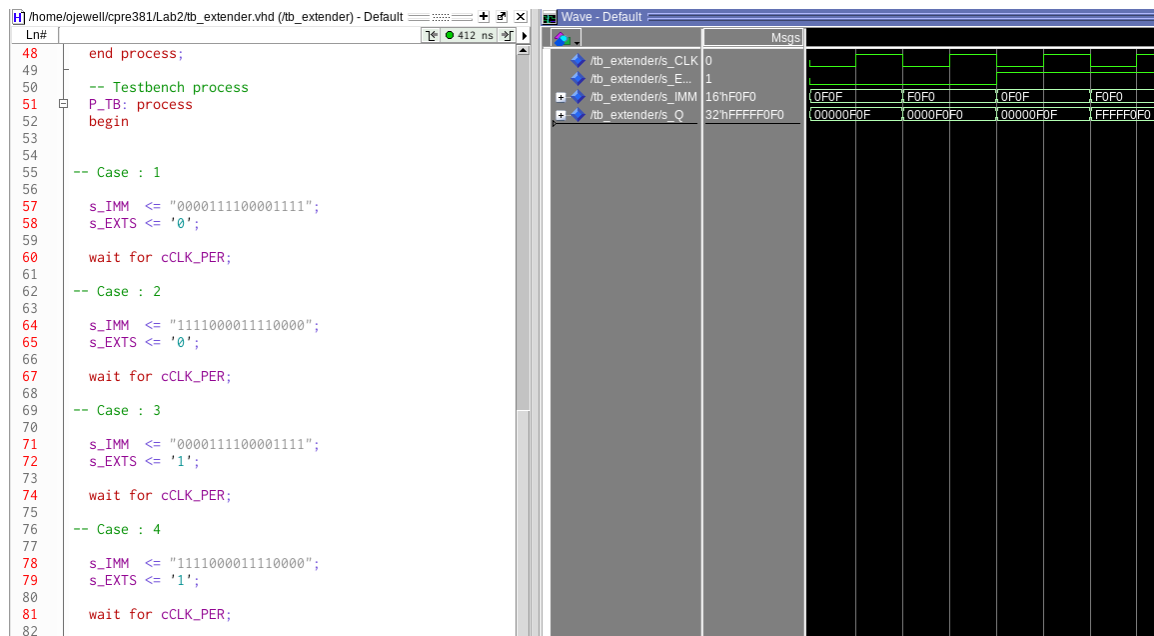


As can be seen in the screenshot the first two test cases 0 extend a number with a 0 and then a 1 in the most significant bit position. Then in the next two cases I sign extend a number with a 0 and a number with a 1 in the most significant bit position.


[Part 6 (a)] what control signals will need to be added to the simple processor from part 2? How do these control signals correspond to the ports on the mem.vhd component analyzed in part 3?

I will need to add a new signal that is the write enable for data memory. This directly corresponds to the write enable of mem.vhd. I will also need the immediate input and the extension type selector for the immediate extender. I also need to take the output of the mini alu and the the output of the memory module and mux these into the register data in port to load from memory or operation. Lastly there will need to be a signal from R[rt] output of register file to data_in of mem.vhd in order to store into memory.

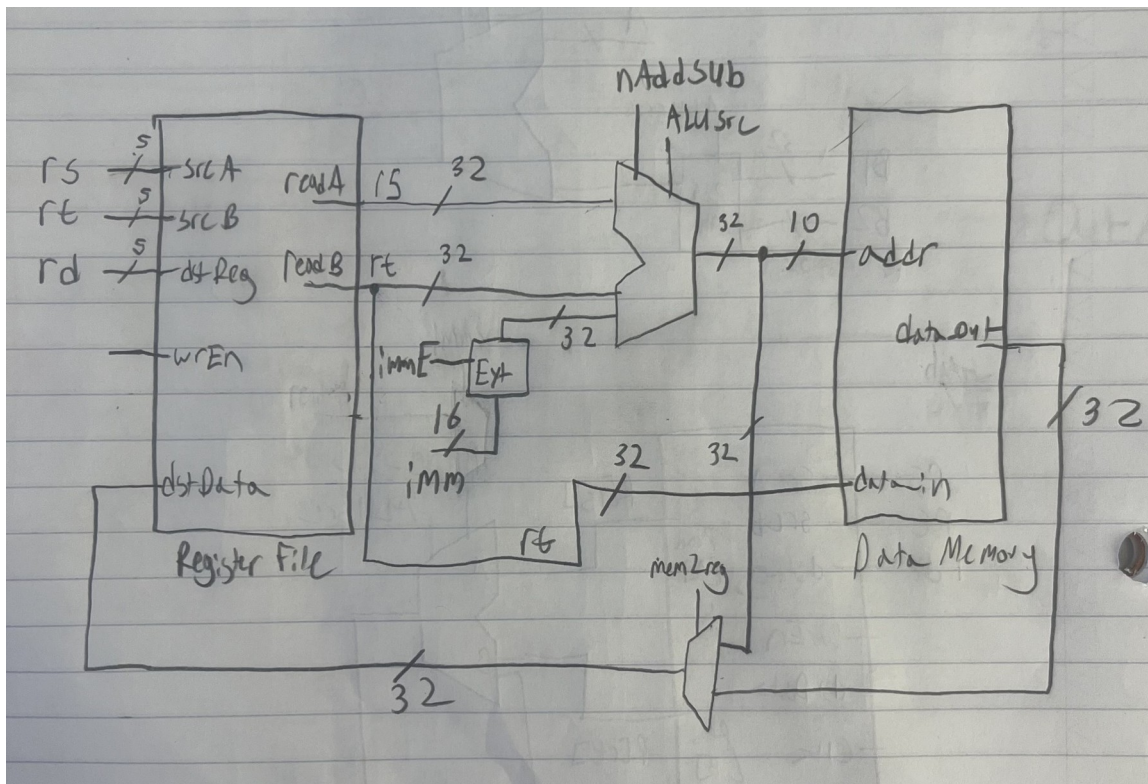[Part 6 (b)] Draw a schematic of a simplified MIPS processor consisting only of the base components used in part 2, the extender component described in part 4, and the data memory from part 3.



[Part 6 (c)] Waveform.

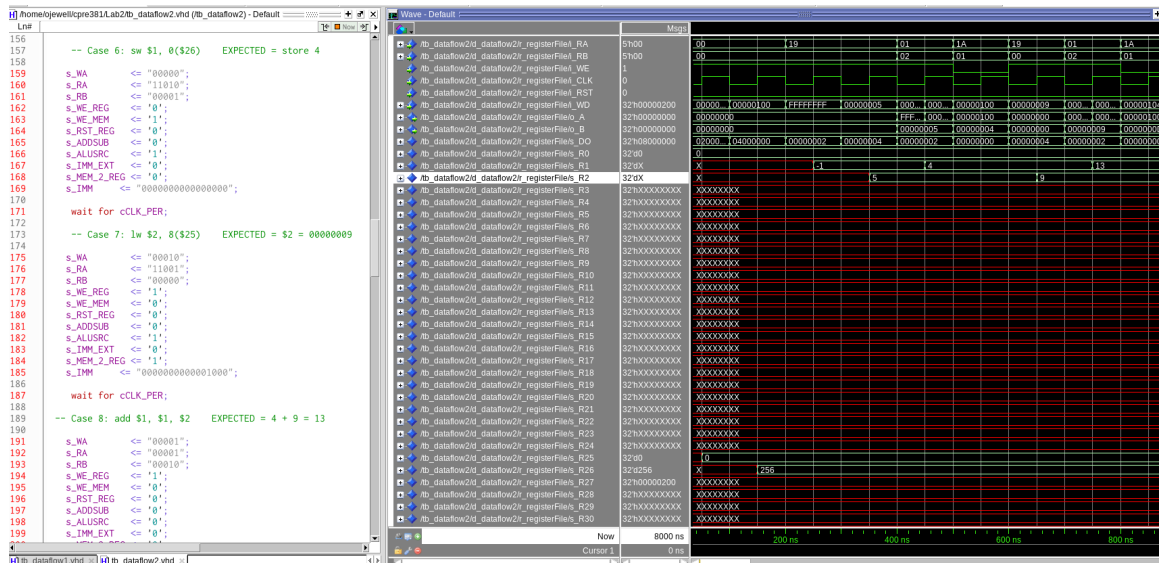

This output is using the actual offset of 4 as specified in the instruction. The next pictures will use offsets of 0,1,2,3,4,5,6 instead of 0,4,8,12,16,20,24.

